




Electronic Circuit II

Negative Feedback


Mifta Nur Farid

30 March 2023


Voltage-Controlled Voltage Source

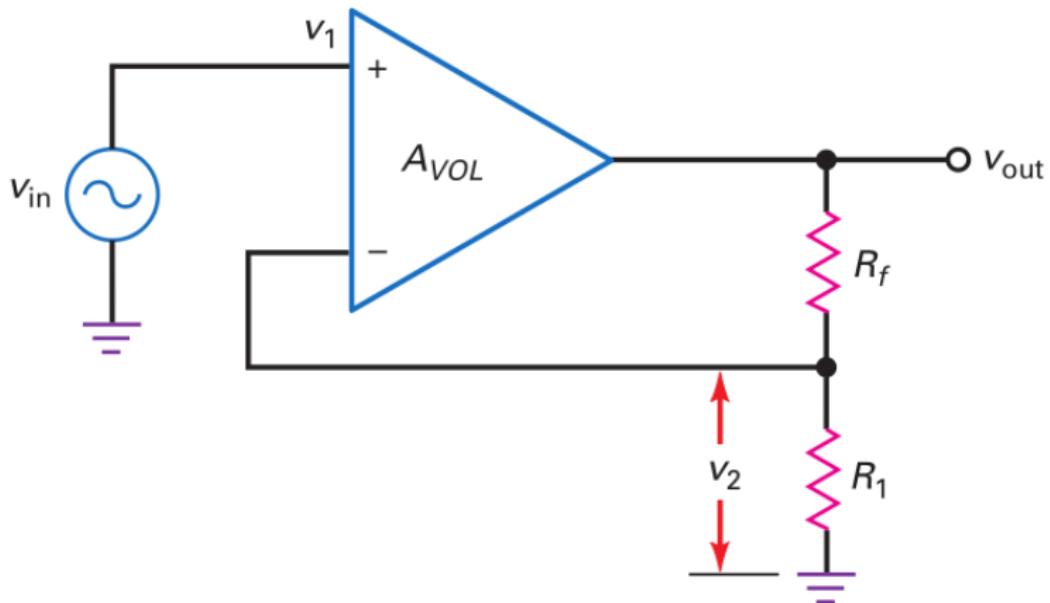

Voltage-Controlled Voltage Source

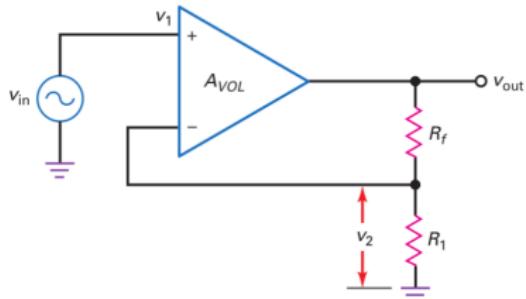


Non-Inverting Amplifier

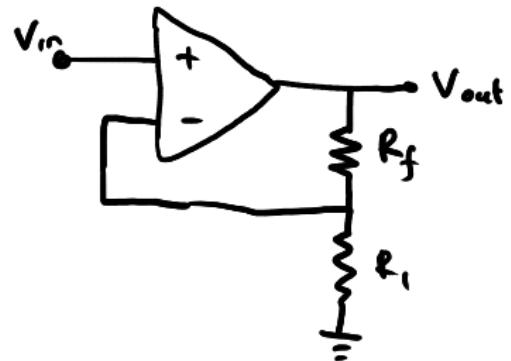


$$V_{out} : \left(\frac{R_f}{R_1} + 1 \right) V_{in}$$


Current-Controlled Voltage Source

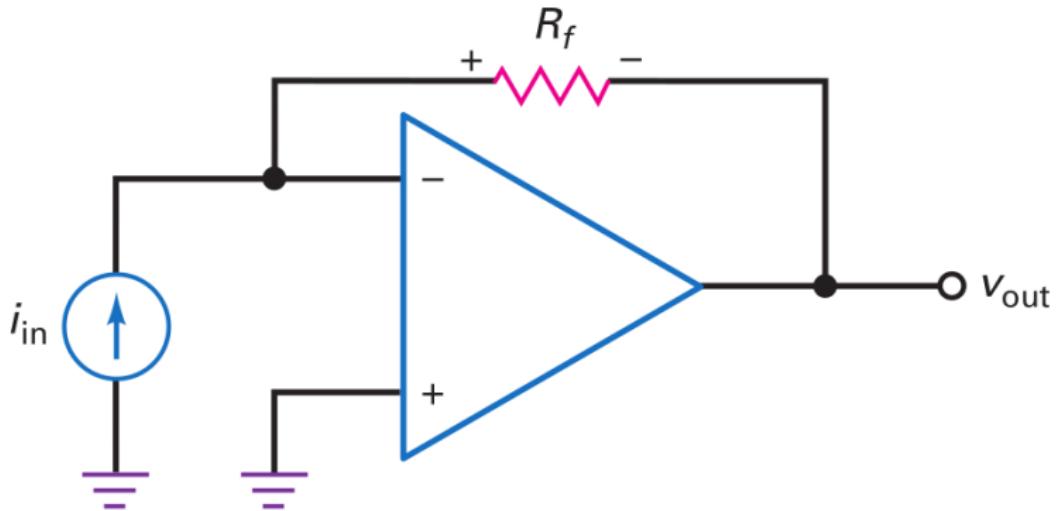

Current-Controlled Voltage Source

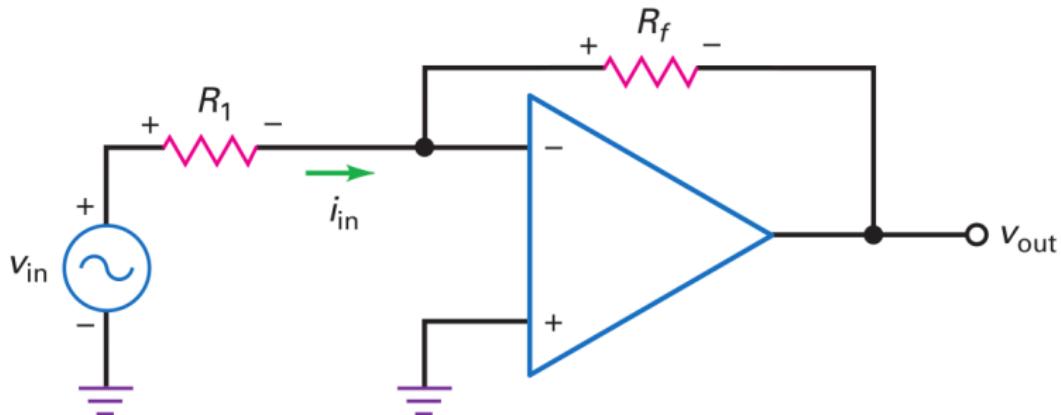

Current-Controlled Voltage Source

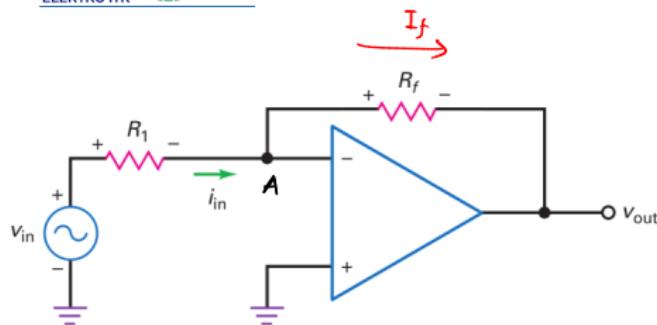


$$I_f = I_{in}$$

$$\frac{V_A - V_{out}}{R_f} = I_{in}$$


$$-V_{out} = I_{in} \cdot R_f$$

$$V_{out} = -I_{in} R_f$$

Voltage-Controlled Current Source

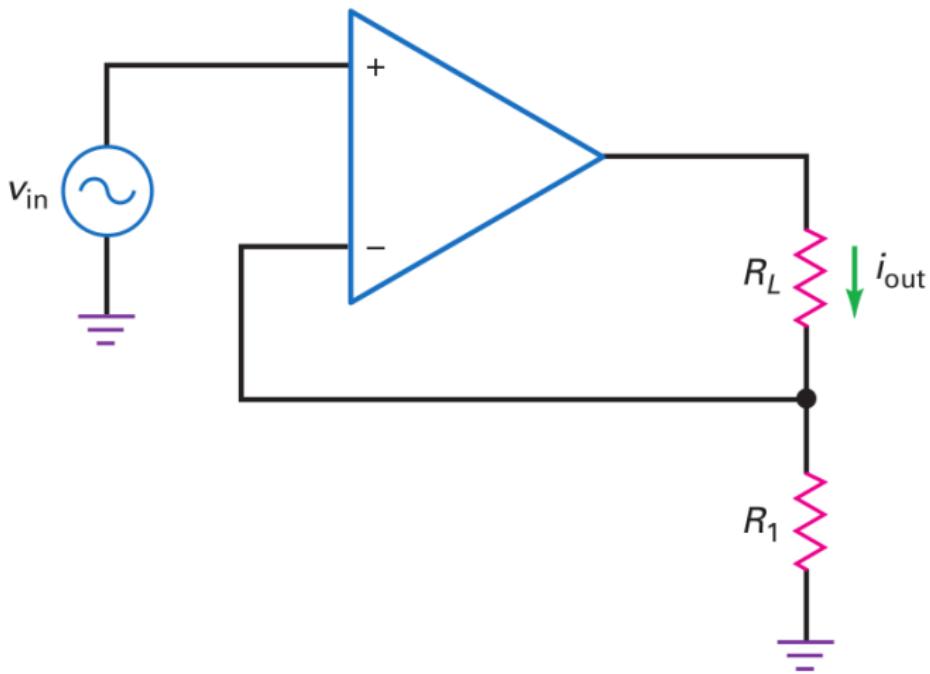


Voltage-Controlled Current Source

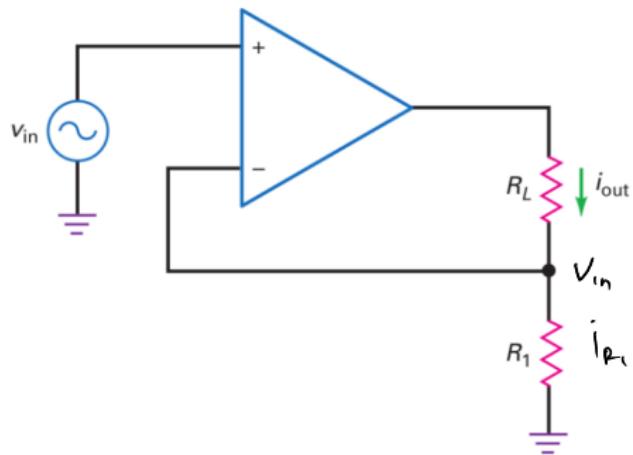


$$\begin{aligned} i_{out} &= i_{R_1} \\ &= \frac{V_{in}}{R_1} \end{aligned}$$

Current-Controlled Current Source

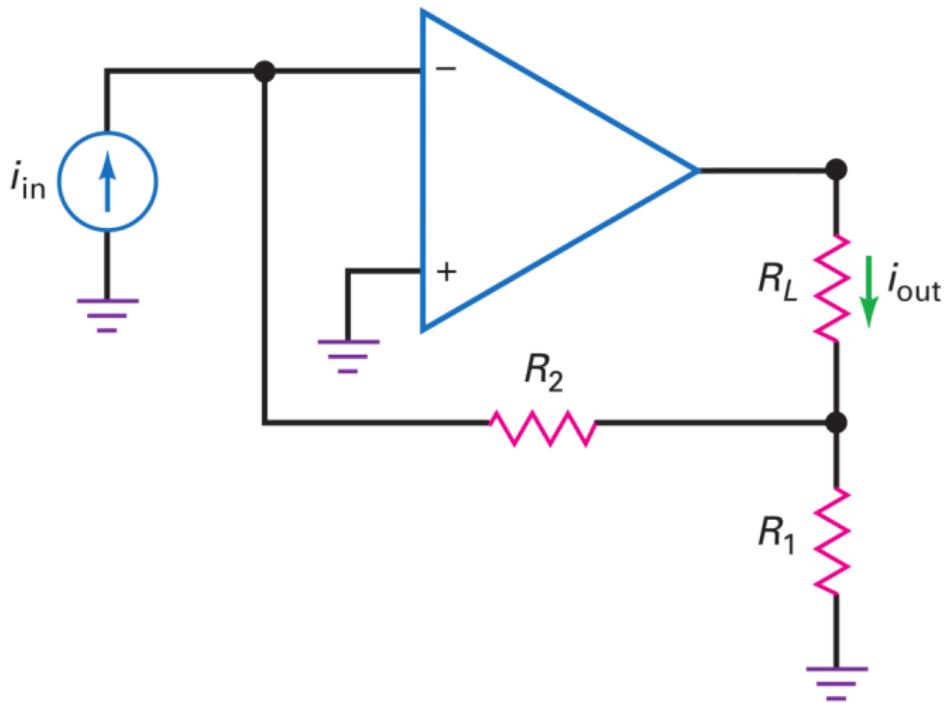

Current-Controlled Current Source

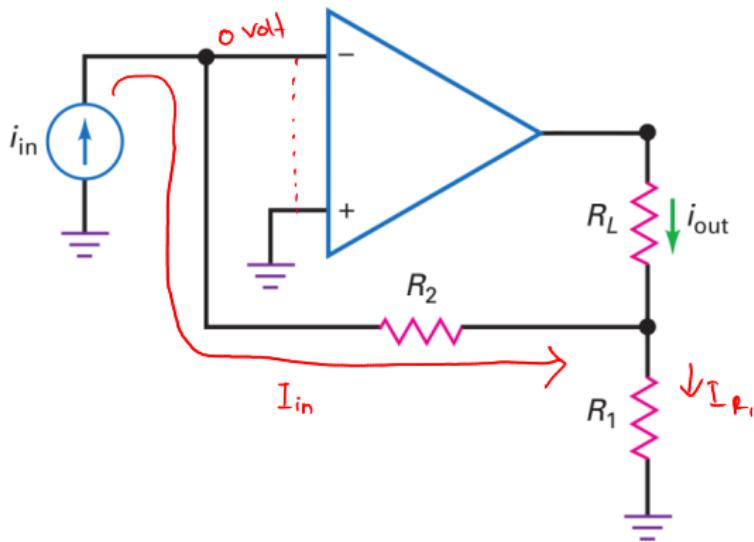

$$\sum V = 0$$

$$I_{in} R_2 + (I_{in} + I_{out}) R_1 = 0$$

$$I_{in} R_2 + I_{in} R_1 + I_{out} R_1 = 0$$

$$I_{in} (R_2 + R_1) + I_{out} R_1 = 0$$

$$- I_{in} \left(\frac{R_2 + R_1}{R_1} \right) = I_{out}$$

$$I_{out} = - \left(\frac{R_2 + R_1}{R_1} \right) I_{in}$$

$$I_{out} = - \left(\frac{R_2}{R_1} + 1 \right) I_{in}$$