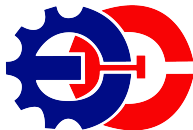


Active Filter Design

TE201414 - Rangkaian Elektronika

Program Studi Teknik Elektro



Institut Teknologi Kalimantan
agung.nursyeha@lecturer.itk.ac.id
miftanurfarid@lecturer.itk.ac.id


June 3, 2025

several things should be specified while designing analog active filter:

- Frequency response bode plot
- Cut off frequency
- Intended attenuation
- Filter order
- Circuit
- Value of the resistance and capacitance

Kind of Filter

approximation digital filter

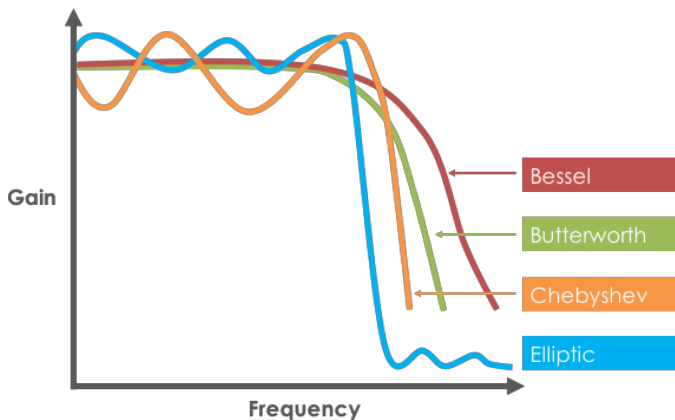

Butterworth filter as approximation for analog filter with op-amp

Filter Order

assume that cut off frequency, and intended attenuation at certain frequency are f_c , A_v , and f respectively.

normalized frequency can be calculated by dividing f to f_c (low-pass filter)

$$\omega = \frac{f}{f_c}$$

and (high-pass filter)

$$\omega = \frac{f_c}{f}$$

filter order with Butterworth attenuation

$$A_v(\omega)_{dB} \leq 10 \log(1 + \omega^{2n})$$

Example 1

Design a filter that have cut off frequency at 500Hz and attenuation -10dB at 1000Hz !

based on case above, the filter required is low pass filter. then:

$$\omega = \frac{f}{f_c} = \frac{1000}{500} = 2$$

Butterworth attenuation filter:

$$A_v(\omega)_{dB} \leq 10\log(1 + \omega^{2n})$$

$$10\text{dB} \leq 10\log(1 + 2^{2n})$$

$$1 \leq \log(1 + 2^{2n})$$

$$10^1 \leq 1 + 2^{2n}$$

$$9 \leq 2^{2n}$$

Example 1

logarithmic basis 2

$$\log_2 9 \leq 2n \rightarrow \frac{\log 9}{\log 2} \geq 2n$$

$$\frac{0.95}{0.301} \leq 2n$$

$$n \geq 3.15$$

filter order to approach the required specification is

$$n = 4$$


find the R-C value, assume that $R = 10k\Omega$:

$$f_c = \frac{1}{2\pi RC}$$

$$500 = \frac{1}{2\pi 10^4 C} \rightarrow C = 3.2 * 10^{-8} F$$


Example 1

Low-pass filter circuit

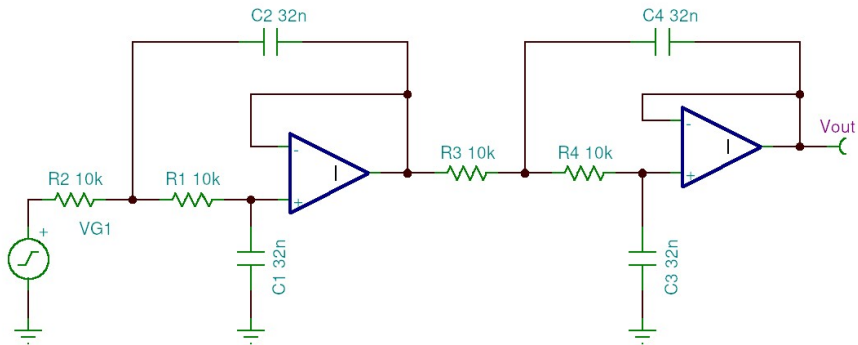


Example 1

Bode plot diagram

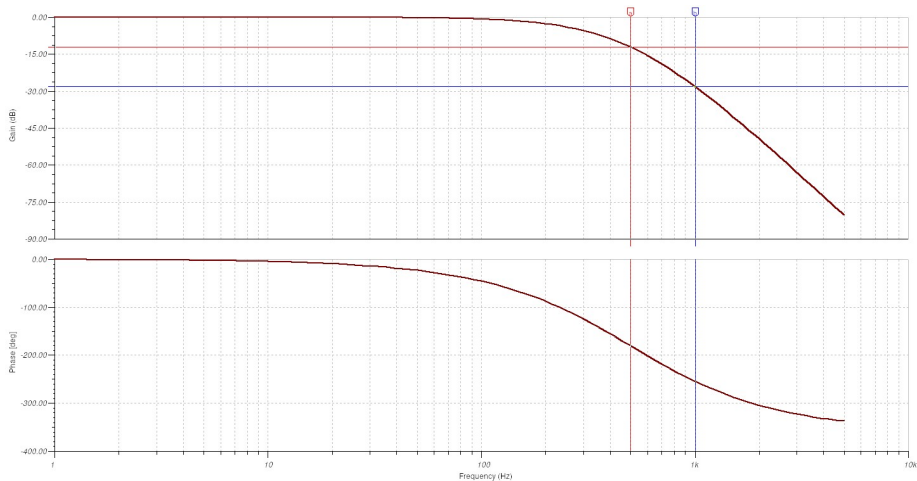

Example 2

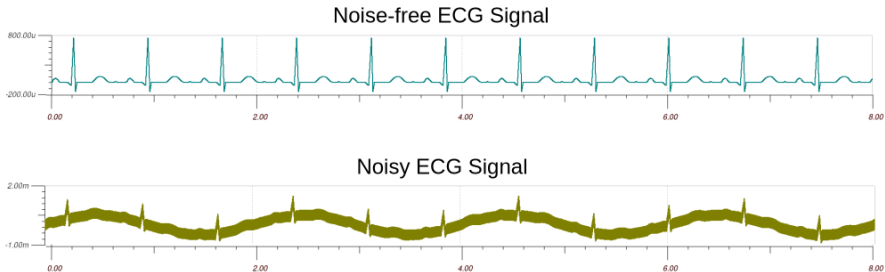

a noisy ecg signal is given above. ecg signal has frequency band between 3 – 10Hz. noises has 2 component, high frequency and low frequency. the frequency of noise are at 1kHz and 0.5Hz. the amplitude of 1kHz noise is 500 μ V peak-peak. 0.5Hz noise is 1mV peak-peak. design a filter circuit that attenuate the HF noise amplitude to 5 μ V peak-peak and LF noise to 10 μ V peak-peak.

Example 2

based on the problem above there are 2 noise components present on ECG signal. filter required for attenuating both noise frequency is band pass filter.

- lower frequency (high pass filter):

filter order:

$$A_v(\omega)_{dB} \leq 10 \log(1 + \omega^{2n})$$

$$A_v(\omega)|_{dB} = 20 \log \frac{V_{out}}{V_{in}} = 20 \log \frac{10 \mu V}{1 mV} = -40 dB$$

$$\omega = \frac{f_c}{f} = \frac{3}{0.5} = 6$$

$$40 \leq 10 \log(1 + 6^{2n})$$

$$4 \leq \log(1 + 6^{2n})$$

$$10^4 \leq 1 + 6^{2n}$$

Example 2

$1 \ll 10^4$, then:

$$10^4 \leq 6^{2n}$$

$$2n \geq \log_6 10^4$$

$$2n \geq \frac{\log 10^4}{\log 6}$$

$$2n \geq \frac{4}{\log 2 + \log 3}$$

$$2n \geq \frac{4}{0.301 + 0.477}$$

$$2n \geq 5.14$$

$$n \geq 2.57$$

filter order required is 3.

Example 2

assume that resistor has same value and capacitor has same value. assume resistor value is $1k\Omega$.

$$f_c = \frac{1}{2\pi RC}$$


$$C = \frac{1}{2\pi R f_c}$$

$$C = \frac{1}{2\pi 10^3 3}$$

$$C = 53\mu F$$

3rd order high pass filter (attenuate frequency lower than 3Hz)

Example 2

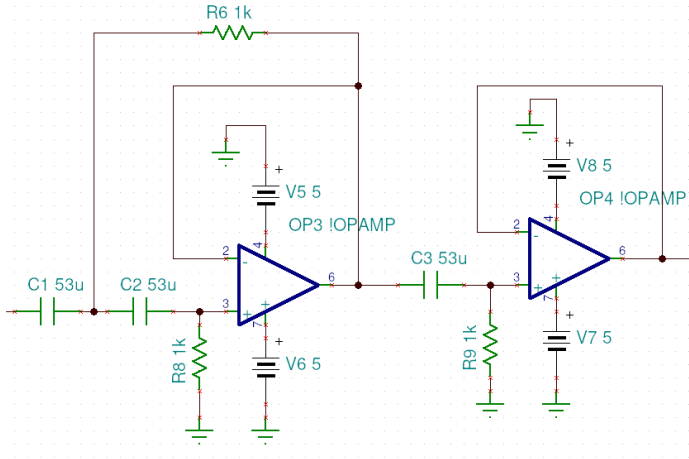

- higher frequency (low pass filter):

Example 2

filter order:

$$A_v(\omega)_{dB} \leq 10 \log(1 + \omega^{2n})$$

$$A_v(\omega)|_{dB} = 20 \log \frac{V_{out}}{V_{in}} = 20 \log \frac{5 \mu V}{500 \mu V} = -40 dB$$

$$\omega = \frac{f}{f_c} = \frac{10^3}{10} = 100$$

$$40 \leq 10 \log(1 + 100^{2n})$$

$$4 \leq \log(1 + 100^{2n})$$

$$10^4 \leq 1 + 100^{2n}$$

$1 \ll 10^4$, then:

$$10^4 \leq 100^{2n}$$

$$2n \geq \frac{\log 10^4}{\log 100}$$

Example 2

$$2n \geq \frac{4}{2}$$

$$n \geq 1$$

filter order required is 1.

assume that resistor has same value and capacitor has same value. assume resistor value is $1k\Omega$.

$$f_c = \frac{1}{2\pi RC}$$


$$C = \frac{1}{2\pi R f_c}$$

$$C = \frac{1}{2\pi 10^4 10}$$

$$C = 15\mu F$$


1st order low pass filter (attenuate frequency higher than 10Hz)

Example 2

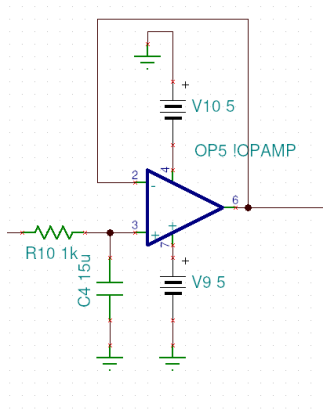


- complete circuit


Example 2

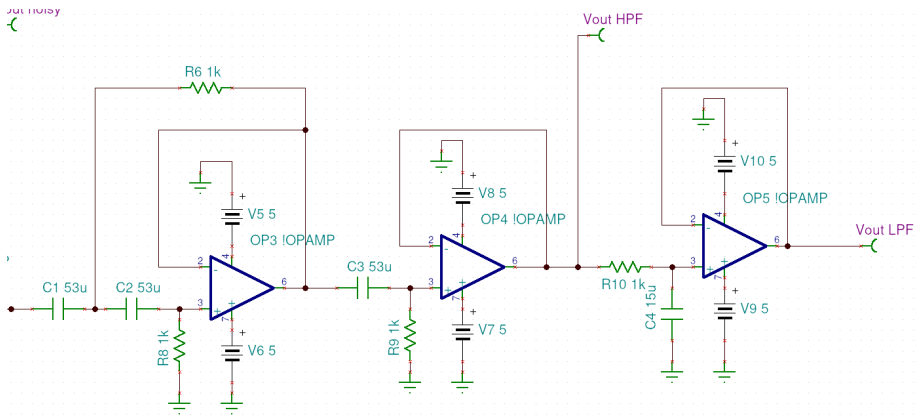

Example 2

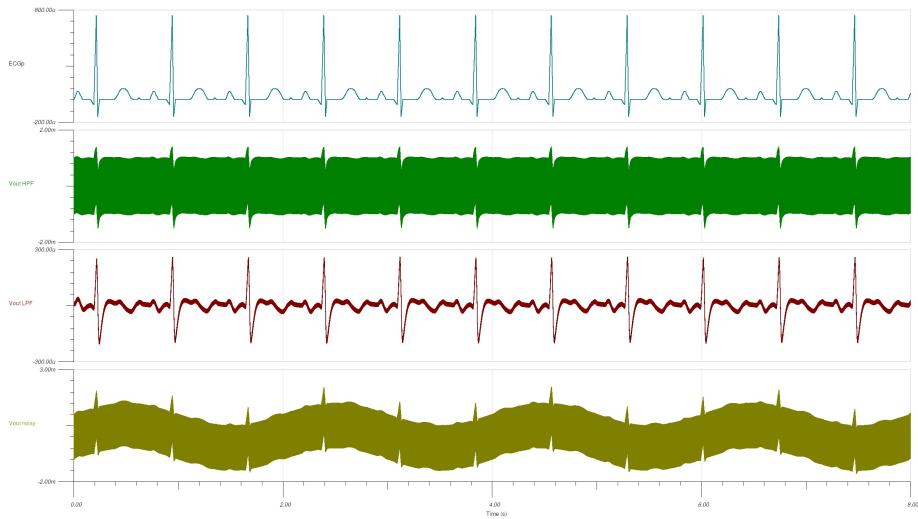

Example 2

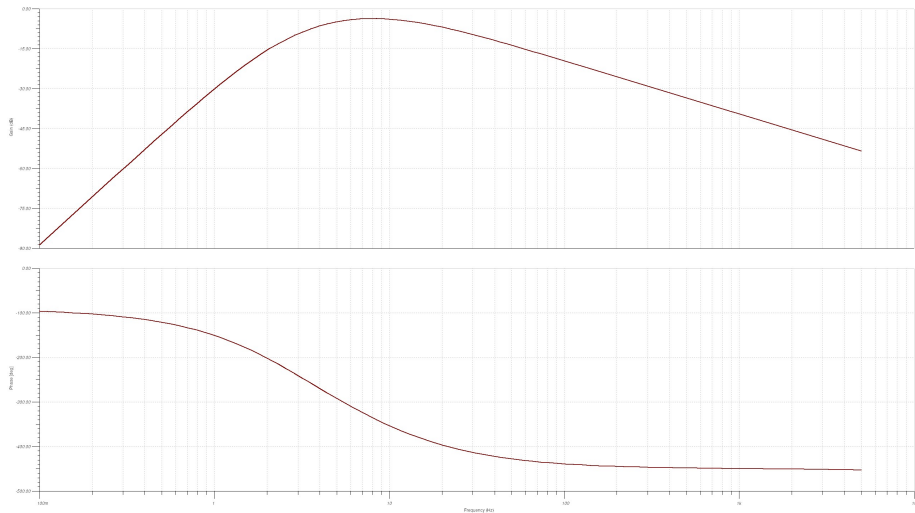

References

Floyd,T.L., Fundamentals of Analog Circuits, Prentice Hall, .

Malvino,A., Electronic Principle, McGrawHill, 2016.

Boylestad, R.L., Nashelsky,L., Electronics Devices and Circuit Theory, Pearson, 2014.

Terima Kasih