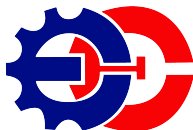


# Operational Amplifier: Amplifier (cont.)

TE201414 - Rangkaian Elektronika 2

Program Studi Teknik Elektro




Institut Teknologi Kalimantan  
*agung.nursyeha@lecturer.itk.ac.id*  
*miftanurfarid@lecturer.itk.ac.id*

March 18, 2025


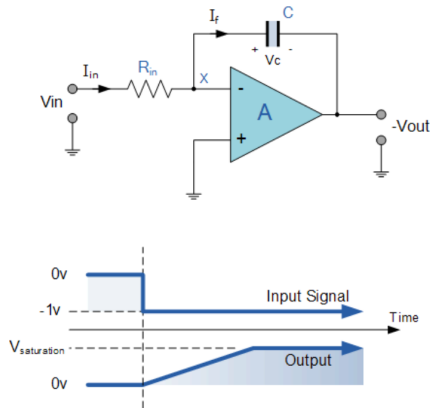
# Integrator

op-amp as integrator is an amplifier where:  
that execute integration operation.



$$V_+ = V_- = 0V$$

$$I_{in} = I_C$$

$$\frac{V_{in}}{R_{in}} = C \frac{\partial V_C}{\partial t}$$


$$\frac{V_{in}}{R_{in}} = C \frac{\partial V_C}{\partial t}$$

$$\partial V_C = \frac{1}{V_{in} R_{in}} V_{in} \partial t$$


$$V_C = \frac{1}{C R_{in}} \int V_{in} \partial t$$

$$V_{out} = -\frac{1}{C R_{in}} \int V_{in} \partial t$$

# Integrator

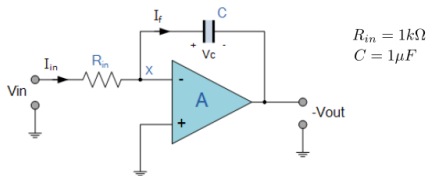
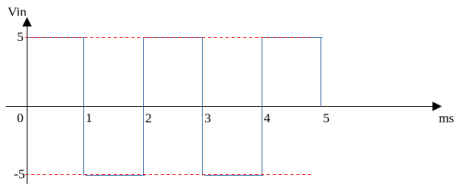
$$V_{in}(t) = \begin{cases} 5v & n < t < (n+1), n = 0, 2, 4, \dots \\ -5v & n < t < (n+1), n = 1, 3, 5, \dots \end{cases}$$



# Integrator

for even  $n$ :


$$V_{out} = -\frac{1}{1k1\mu F} \int 5\partial t$$

$$V_{out} = -1000 * 5t$$


for odd  $n$ :

$$V_{out} = -\frac{1}{1k1\mu F} \int -5\partial t$$


$$V_{out} = 1000 * 5t$$

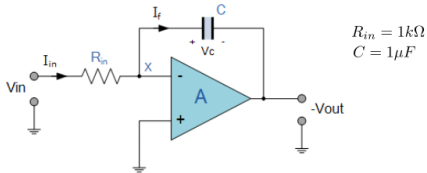
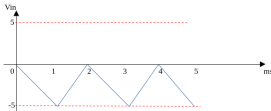
$$V_{in}(t) = \begin{cases} -5000t + c & n < t < (n+1), n = 0, 2, 4, \dots \\ -5000t + c & n < t < (n+1), n = 1, 3, 5, \dots \end{cases}$$



# Differentiator

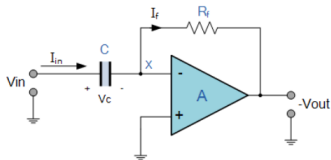


op-amp as differentiator is an amplifier that execute differentiation operation.  
where:

$$V^{+} = V^{-} = 0V$$

$$I_{in} = I_C$$


$$C \frac{\partial V_{in}}{\partial t} = - \frac{V_{out}}{R_f}$$
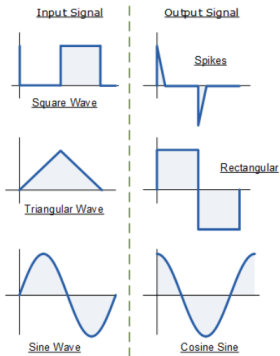
$$V_{out} = -R_f C \frac{\partial V_{in}}{\partial t}$$



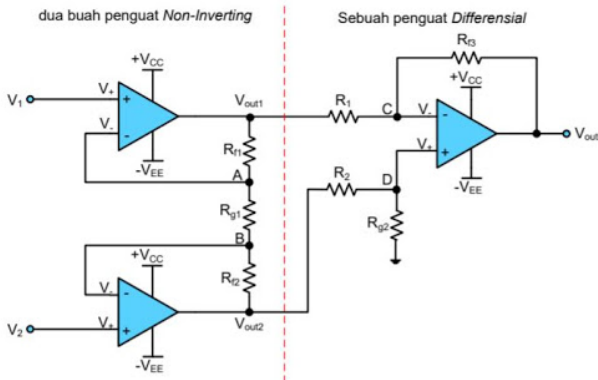
# Penguat Instrumentasi

instrumentation amplifier is most-commonly used for amplify signal in industrial, biomedical, etc. the advantages of using instrumentation amplifier is high input impedance. high input impedance makes sure that all signal transmitted being dissipated by the circuit.



# Penguat Instrumentasi

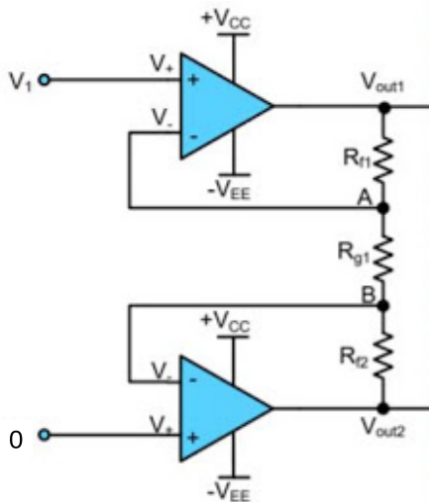

$V_{out1}$  output is non-inverting from  $V_1$ :


$$V_{out1} = \left(1 + \frac{R_{f1}}{R_{g1}}\right) V_1$$

$V_{out2}$  output is inverting from  $V_1$ :

$$V_{out2} = -\frac{R_{f2}}{R_{g1}} V_1$$



# Penguat Instrumentasi

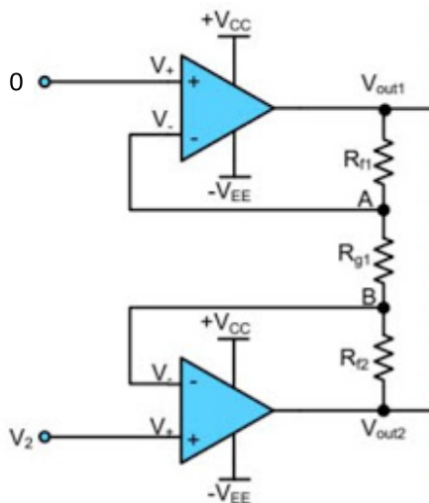

$V_{out1}$  output is inverting from  $V_2$ :


$$V_{out1} = -\frac{R_{f1}}{R_{g1}} V_2$$

$V_{out2}$  output is non-inverting from  $V_2$ :

$$V_{out2} = \left(1 + \frac{R_{f2}}{R_{g1}}\right) V_2$$

# Penguat Instrumentasi

Sebuah penguat *Differential*

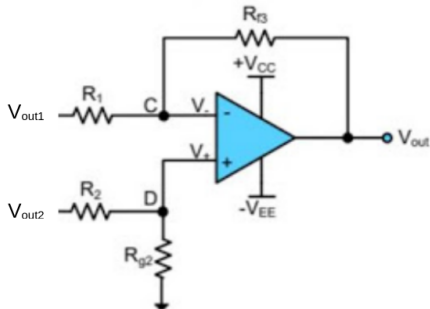

$$V_{out1} = \left(1 + \frac{R_{f1}}{R_{g1}}\right) V_1 - \frac{R_{f1}}{R_{g1}} V_2$$

$$V_{out2} = \left(1 + \frac{R_{f2}}{R_{g1}}\right) V_2 - \frac{R_{f2}}{R_{g1}} V_1$$

differential amplifier:

# References

Floyd,T.L., Fundamentals of Analog Circuits, Prentice Hall, .

Malvino,A., Electronic Principle, McGrawHill, 2016.

Boylestad, R.L., Nashelsky,L., Electronics Devices and Circuit Theory, Pearson, 2014.

Terima Kasih