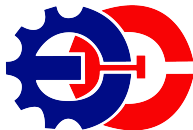


Active Filter

TE201414 - Rangkaian Elektronika 2

Program Studi Teknik Elektro




Institut Teknologi Kalimantan
agung.nursyeha@lecturer.itk.ac.id
agung.nursyeha@lecturer.itk.ac.id

April 14, 2025

Filter



Is a circuit which has function to block and pass signal in certain range of frequency. type of filter can be classified as:

- Passive filter
- Active filter

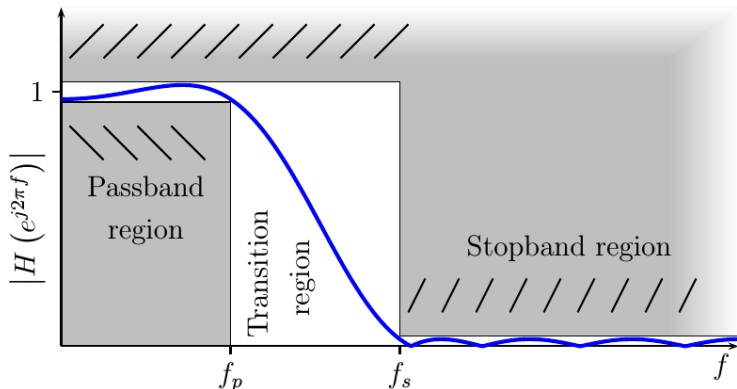


Filter Pasif

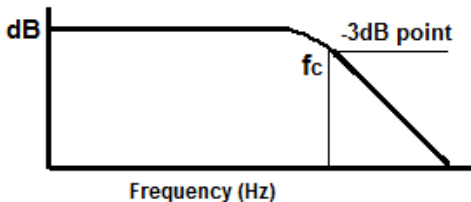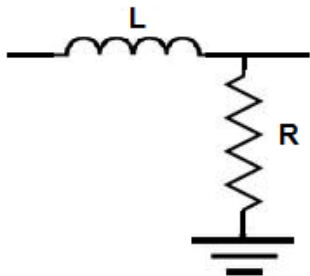terdiri atas rangkaian RC, RL, RLC, contoh filter pasif low-pass dari rangkaian RL:




Filter Aktif

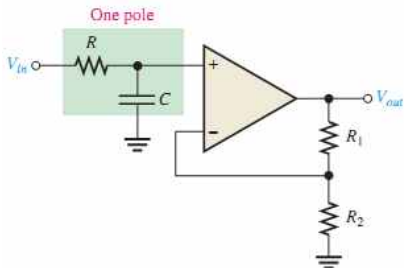Rangkaian filter menggunakan operasional amplifier.
contoh filter aktif low-pass:



(a)

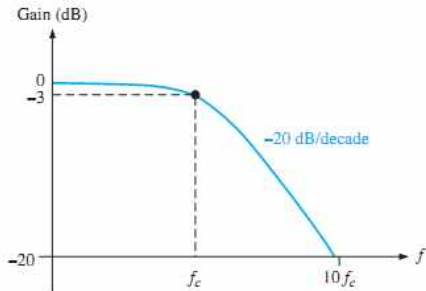


(b)

Keuntungan Filter Aktif


Beberapa keuntungan filter aktif:

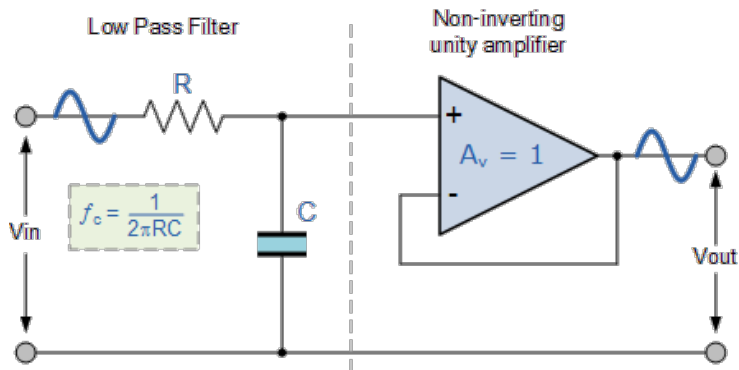- Gain filter dapat diatur.
- Impedansi input tinggi, sehingga tidak mempengaruhi rangkaian sebelumnya.



Filter Aktif Orde 1: Low-pass

Active low-pass filter orde 1:

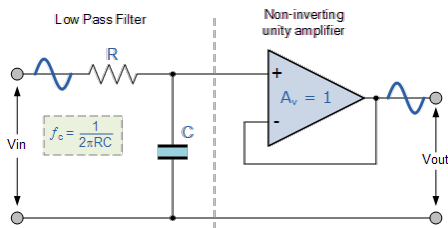

$$V_C = \frac{-jX_C}{-jX_C + R} V_{in}$$

$$V_o = V_C$$

$$\frac{V_o}{V_{in}} = \frac{1}{1 + j\frac{R}{X_C}}$$

Frekuensi cut off ketika $\frac{V_o}{V_{in}} = -3dB$ atau $\frac{1}{\sqrt{2}}$, maka

$$\frac{1}{\sqrt{2}} = \frac{1}{1 + j\frac{R}{X_C}}$$

$X_C = \frac{1}{2\pi fC}$, maka

$$\frac{1}{\sqrt{2}} = \frac{1}{1 + j2\pi fRC}$$

$$f_c = \frac{1}{2\pi RC}$$


Filter Aktif Orde 1: Low-pass

Penguatan tegangan A_v pada untuk setiap frekuensi

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1}{1 + j \frac{f}{f_c}} = \frac{1}{\sqrt{1^2 + \left(\frac{f}{f_c}\right)^2}}$$


Pergeseran fasa
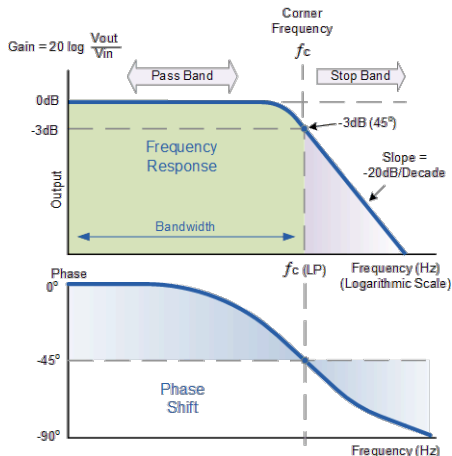
$$\theta = \frac{0^\circ}{\tan^{-1}\left(\frac{f}{f_c}\right)}$$



Filter Aktif Orde 1: High-pass

Active high-pass filter orde 1:

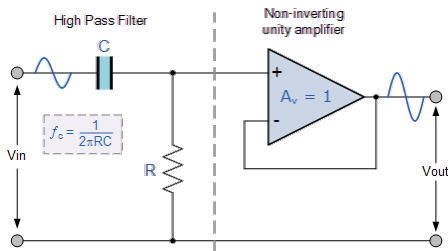

$$V_C = \frac{R}{-jX_C + R} V_{in}$$

$$V_o = V_C$$

$$\frac{V_o}{V_{in}} = \frac{1}{1 + j\frac{X_C}{R}}$$

Frekuensi cut off ketika $\frac{V_o}{V_{in}} = -3dB$
atau $\frac{1}{\sqrt{2}}$, maka

$$\frac{1}{\sqrt{2}} = \frac{1}{1 + j\frac{X_C}{R}}$$


$X_C = \frac{1}{2\pi fC}$, maka

$$\frac{1}{\sqrt{2}} = \frac{1}{1 + j/2\pi fRC}$$

$$f_c = \frac{1}{2\pi RC}$$

Filter Aktif Orde 1: High-pass
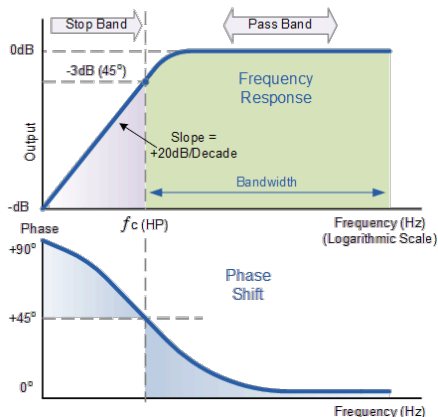
$$\text{Gain (dB)} = 20 \log \frac{V_{out}}{V_{in}}$$




Penguatan tegangan A_v pada untuk setiap frekuensi

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1}{1 + j\frac{f_c}{f}} = \frac{1}{\sqrt{1^2 + \left(\frac{f_c}{f}\right)^2}}$$

Pergeseran fasa

$$\theta = \frac{0^\circ}{\tan^{-1}\left(\frac{f_c}{f}\right)}$$


Cascaded Filter

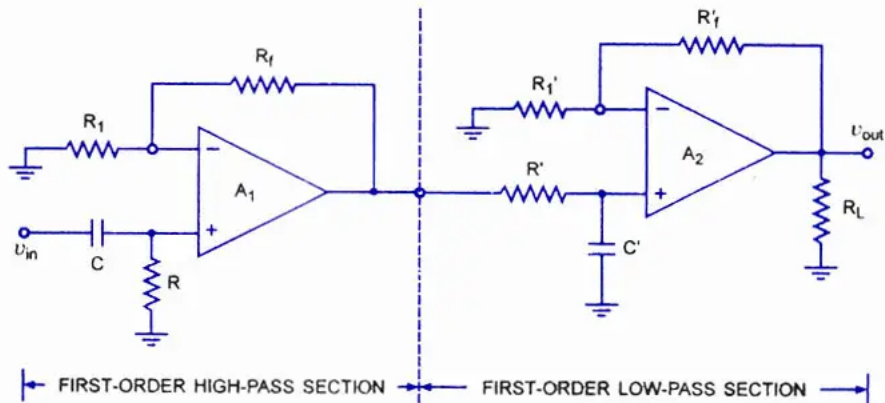


Circuit Diagram

Wide Band Pass Filter

Cascaded Filter

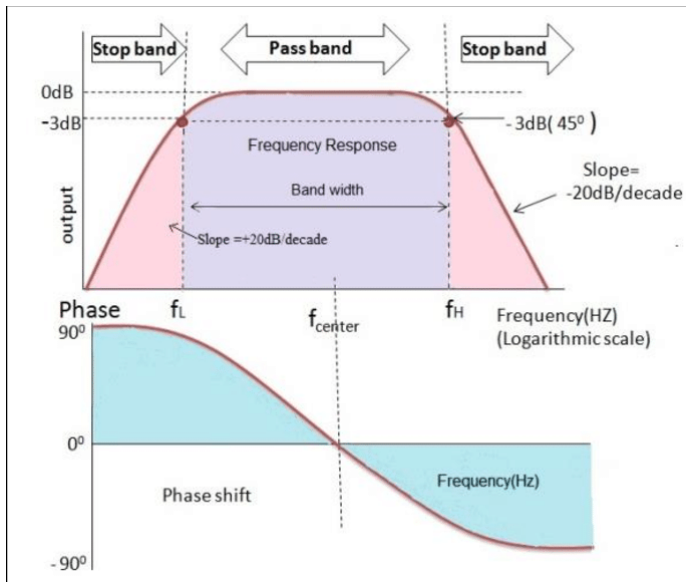

Contoh

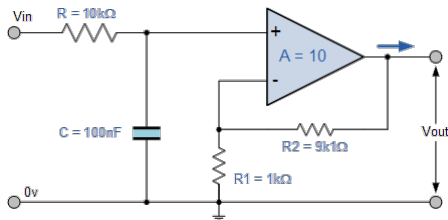


Tentukan!

- Frekuensi cut off (f_c)
- Penguatan tegangan (A_v) dan pergeseran fasa apabila $f = 0.1f_c$
- Penguatan tegangan (A_v) dan pergeseran fasa apabila $f = 10f_c$
- Bode plot frekuensi

Filter Order

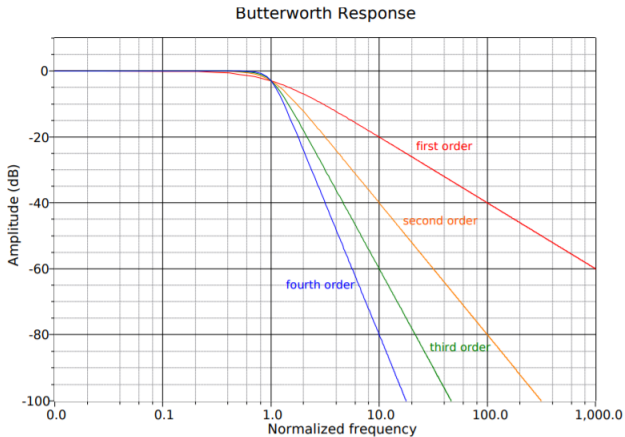
Pengaruh orde filter terhadap respon frekuensi




Ideal Filter

Respon filter ideal


Low-pass filter

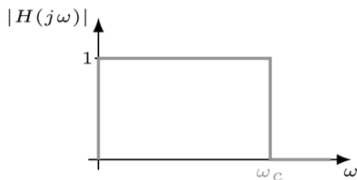


High-pass filter

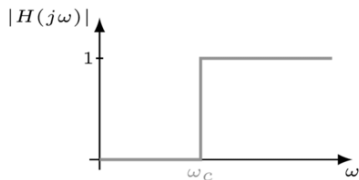

Band-pass filter

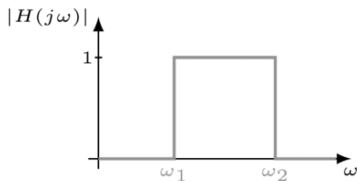


Band-stop filter

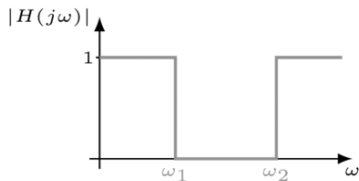

Filter Aktif Orde 2: Low-pass


Active low-pass filter orde 2:

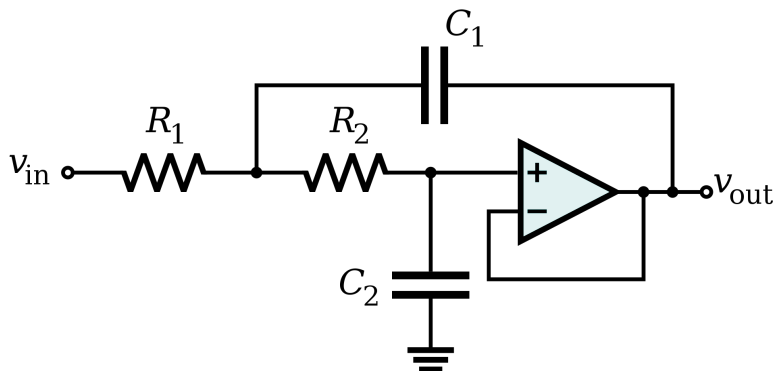

$$f_c = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

Filter Aktif Orde 2: High-pass

Active high-pass filter orde 2:

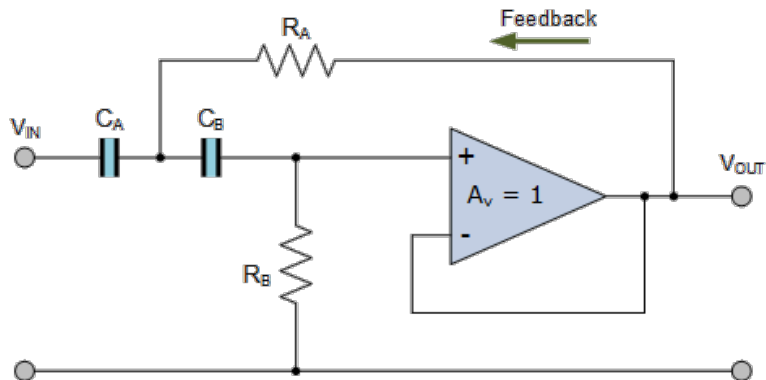


$$f_c = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

Aplikasi Filter Aktif


10-band equalizer



Aplikasi Filter Aktif


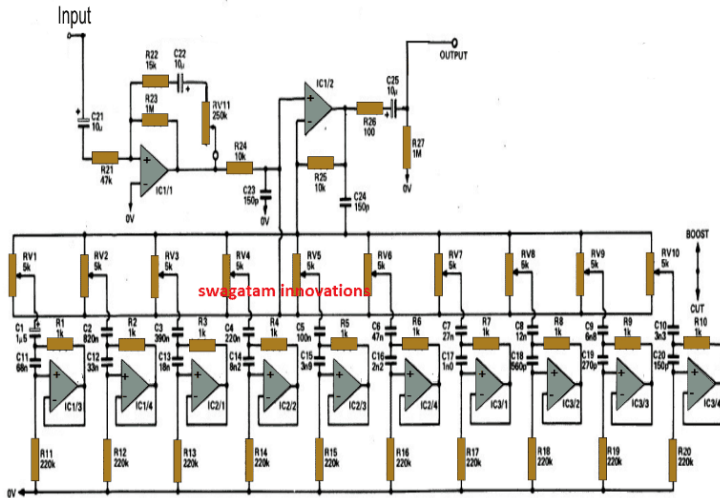


Notch filter ECG

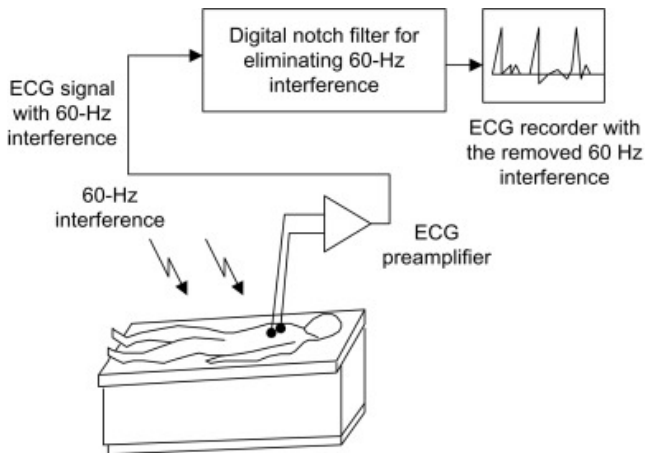

ECG filter

Aplikasi Filter Aktif

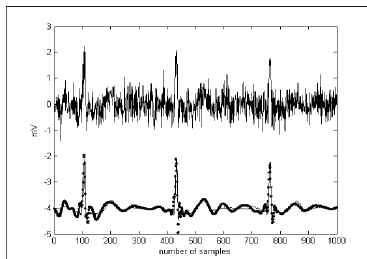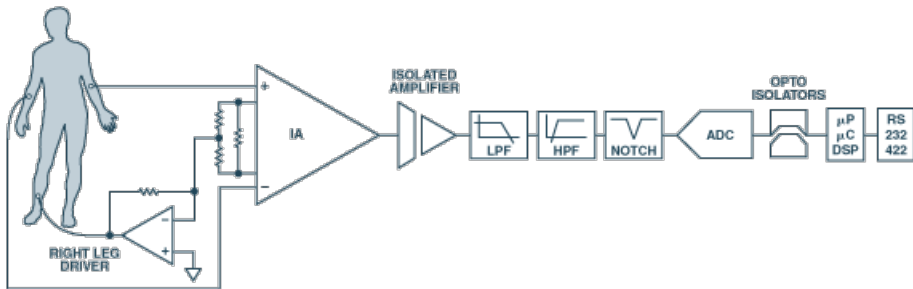

References

Floyd,T.L., Fundamentals of Analog Circuits, Prentice Hall, .

Malvino,A., Electronic Principle, McGrawHill, 2016.

Boylestad, R.L., Nashelsky,L., Electronics Devices and Circuit Theory, Pearson, 2014.

Terima Kasih