RANGKAIAN ELEKTRONIKA II

Negative Feedback



Mifta Nur Farid, S.T., M.T. miftanurfarid@lecturer.itk.ac.id

Teknik Elektro Institut Teknologi Kalimantan Balikpapan, Indonesia

Maret 10, 2021

Sub-CPMK



Mahasiswa mampu memperbandingkan keempat jenis negative feedback (C5, P4, A4)

Bahan Kajian



- 1. Konsep dasar negative feedback;
- 2. VCVS voltage gain;
- 3. ICVS amplifier;
- 4. VCIS amplifier;
- 5. ICIS amplifier.





- lacktriangle Negative feeback pertama ightarrow menstabilkan voltage gain, meningkatkan impedansi input, menurunkan impedansi output
- lacksquare Dengan adanya transistor & op amps ightarrow bertambah 3 jenis negative feedback

Ide Dasar



■ Input dan output negative feedback amplifier bisa berupa tegangan maupun arus

Konverter



content...

Diagram



content...



Voltage-Controlled Voltage Source (VCVS)



Current-Controlled Voltage Source (ICVS)



Voltage-Controlled Current Source (VCIS)



Current-Controlled Current Source (ICIS)



TERIMA KASIH