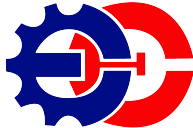


Active Filter

TE201414 - Rangkaian Elektronika 2

Program Studi Teknik Elektro




Institut Teknologi Kalimantan
agung.nursyeha@lecturer.itk.ac.id
miftanurfarid@lecturer.itk.ac.id


May 18, 2025

Second Order Active Filter: Sallen-Key Topology

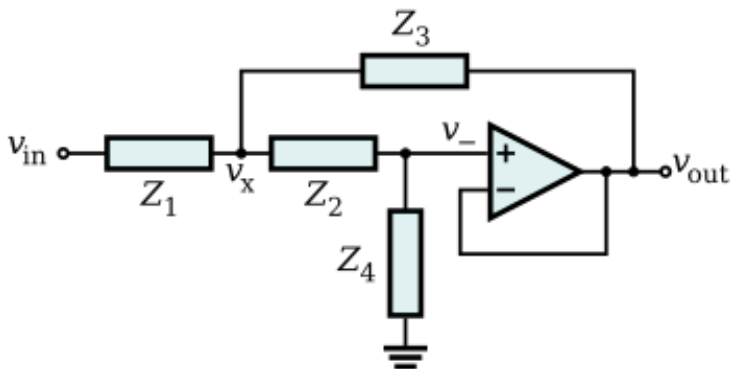
the Sallen-Key topology is an electronic filter topology used to implement second-order active filters that is particularly valued for its simplicity.



Second Order Low Pass Filter

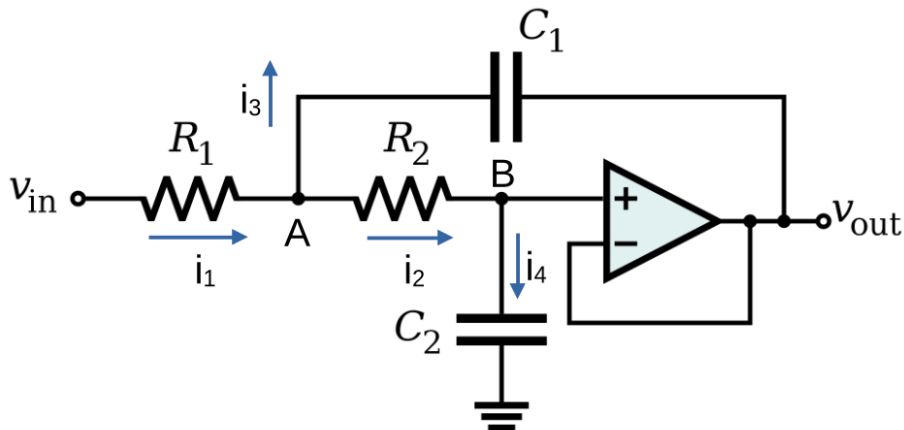

Second Order Low Pass Filter

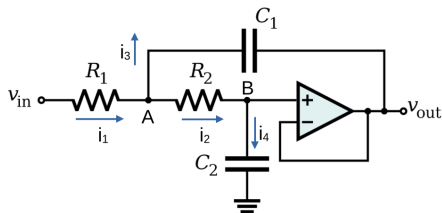

$$I_2 = \frac{V_A - V_B}{R_2} = \frac{V_A - V_{out}}{R_2}$$

review node B:

$$I_2 = I_4 = j\omega C_2 V_{out}$$

V_{out} is similar with voltage at node B V_B , then:

$$I_4 = \frac{V_{out}}{X_{C2}} = j\omega C_2 V_{out}$$

$$\frac{V_A - V_{out}}{R_2} = j\omega C_2 V_{out}$$

$$V_A = V_{out} + j\omega R_2 C_2 V_{out}$$

$$I_3 = \frac{V_A - V_{out}}{X_{C1}} = (V_A - V_{out})j\omega C_1$$

Second Order Low Pass Filter

$$I_3 = (V_{out} + j\omega R_2 C_2 V_{out} - V_{out})j\omega C_1$$

$$I_3 = -\omega^2 R_2 C_1 C_2 V_{out}$$

review node A:

$$I_1 = I_2 + I_3$$

$$I_1 = \frac{V_{in} - V_A}{R_1}$$

$$\frac{V_{in} - V_A}{R_1} = j\omega C_2 V_{out} + (-\omega^2 R_2 C_1 C_2 V_{out})$$

$$V_{in} = V_A + j\omega R_1 C_2 V_{out} - \omega^2 R_1 R_2 C_1 C_2 V_{out}$$

$$V_{in} = V_{out} + j\omega R_2 C_2 V_{out} + j\omega R_1 C_2 V_{out} - \omega^2 R_1 R_2 C_1 C_2 V_{out}$$

$$V_{in} = V_{out}(1 - \omega^2 R_1 R_2 C_1 C_2 + j\omega C_2(R_1 + R_2))$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 - \omega^2 R_1 R_2 C_1 C_2 + j\omega C_2(R_1 + R_2)}$$

Second Order Low Pass Filter

Every 1 order increase in the lowpass filter will shift the phase by -45 degrees, so it be -90 degrees phase shift for second order low pass filter at cut off frequency. the real value for -90 degree phase is zero, then

$$0 = 1 - \omega_c^2 R_1 R_2 C_1 C_2$$

$$\omega_c^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$f_c = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

to find signal amplification of bode plot: assume that $R_1 = R_2 = R$ and $C_1 = C_2 = C$

$$C = \frac{1}{\omega_c R}$$

Second Order Low Pass Filter

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 - \omega^2 R R \frac{1}{\omega_c R} \frac{1}{\omega_c R} + j\omega \frac{1}{\omega_c R} (2R)}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 - \left(\frac{\omega}{\omega_c}\right)^2 + j2\frac{\omega}{\omega_c}}$$


$$|A_v|_{\omega} = \frac{1}{\sqrt{\left(2\frac{\omega}{\omega_c}\right)^2 + \left(1 - \left(\frac{\omega}{\omega_c}\right)^2\right)^2}}$$

to find phase shift of bode plot:


$$\phi = 0 - \arctan \frac{2\frac{\omega}{\omega_c}}{1 - \left(\frac{\omega}{\omega_c}\right)^2}$$

Second Order Low Pass Filter

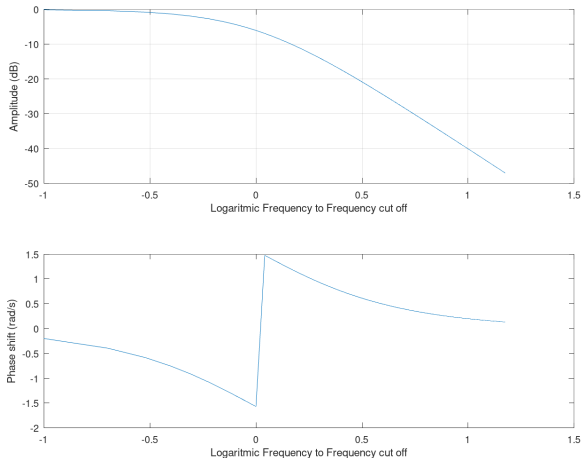
Frequency response of second order active low filter.



Second Order High Pass Filter

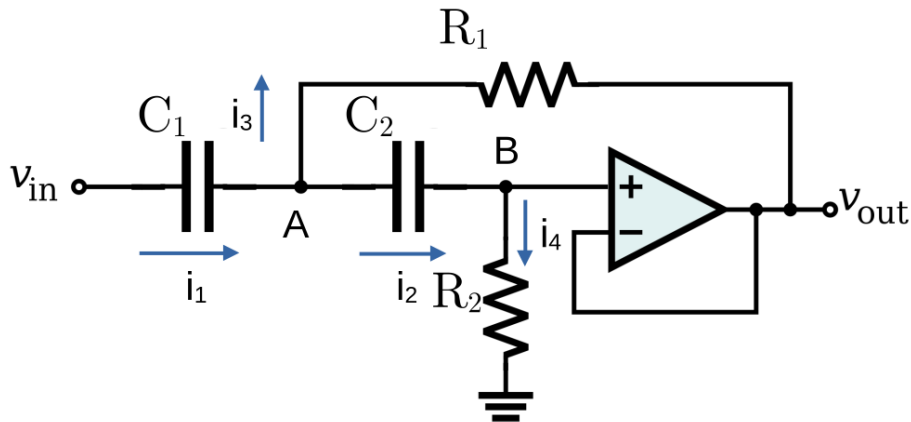

Second Order High Pass Filter

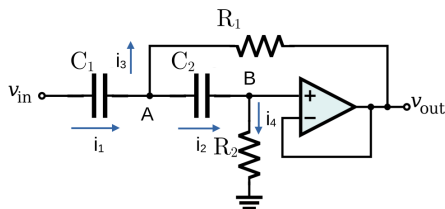

$$I_2 = \frac{V_A - V_B}{X_{C_2}} = j\omega C_2(V_A - V_{out})$$

review node B:

$$I_2 = I_4 = \frac{V_{out}}{R_2}$$

V_{out} is similar with voltage at node B V_B , then:

$$I_4 = \frac{V_{out}}{R_2}$$

$$j\omega C_2(V_A - V_{out}) = \frac{V_{out}}{R_2}$$

$$j\omega R_2 C_2(V_A - V_{out}) = V_{out}$$

$$V_A = V_{out} + \frac{V_{out}}{j\omega R_2 C_2}$$

Second Order High Pass Filter

$$I_3 = \frac{V_A - V_{out}}{R_1}$$

review node A:

$$I_1 = I_2 + I_3$$

$$I_1 = \frac{V_{in} - V_A}{X_{C1}}$$

$$\frac{V_{in} - V_A}{X_{C1}} = \frac{V_A - V_{out}}{X_{C2}} + \frac{V_A - V_{out}}{R_1}$$

$$\frac{V_{in} - (\frac{V_{out}}{j\omega R_2 C_2} + V_{out})}{\frac{1}{j\omega C_1}} = \frac{V_{out}}{j\omega R_2 C_2} + V_{out} - V_{out} \frac{1}{j\omega C_2} + \frac{(\frac{V_{out}}{j\omega R_2 C_2} + V_{out})}{R_1}$$

$$\frac{V_{in} - (\frac{V_{out}}{j\omega R_2 C_2} + V_{out})}{\frac{1}{j\omega C_1}} = \frac{\frac{V_{out}}{j\omega R_2 C_2}}{\frac{1}{j\omega C_2}} + \frac{\frac{V_{out}}{j\omega R_2 C_2}}{R_1}$$

Second Order High Pass Filter

$$\frac{V_{in} - \left(\frac{V_{out}}{j\omega R_2 C_2} + V_{out} \right)}{\frac{1}{j\omega C_1}} = \frac{V_{out}}{R_2} + \frac{V_{out}}{j\omega R_1 R_2 C_2}$$

$$V_{in} - \frac{V_{out}}{j\omega R_2 C_2} - V_{out} = \frac{V_{out}}{j\omega R_2 C_1} + \frac{V_{out}}{j\omega^2 R_1 R_2 C_1 C_2}$$

$$V_{in} = V_{out} - \frac{V_{out}}{\omega^2 R_1 R_2 C_1 C_2} + \frac{V_{out}}{j\omega R_2 C_1} + \frac{V_{out}}{j\omega R_2 C_2}$$

$$\frac{V_{out}}{V_{in}} = 1 - \omega^2 R_1 R_2 C_1 C_2 + j\omega R_2 C_2 + j\omega R_2 C_1$$

Every 1 order increase in the lowpass filter will shift the phase by +45 degrees, so it be +90 degrees phase shift for second order low pass filter at cut off frequency. the real value for +90 degree phase is zero, then

Second Order High Pass Filter

$$0 = 1 - \omega_c^2 R_1 R_2 C_1 C_2$$

$$\omega_c^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$f_c = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

to find signal amplification of bode plot: assume that $R_1 = R_2 = R$ and $C_1 = C_2 = C$

$$C = \frac{1}{\omega_c R}$$

$$\frac{V_{out}}{V_{in}} = 1 - \omega^2 R^2 \left(\frac{1}{\omega_c R}\right)^2 + 2j\omega R \frac{1}{\omega_c R}$$

$$\frac{V_{out}}{V_{in}} = 1 - \left(\frac{\omega}{\omega_c}\right)^2 + 2j\frac{\omega}{\omega_c}$$

Second Order High Pass Filter


$$|A_V|_{\omega} = \sqrt{(2\frac{\omega}{\omega_c})^2 + (1 - (\frac{\omega}{\omega_c})^2)^2}$$

to find phase shift of bode plot:


$$\phi = 0 + \arctan \frac{2\frac{\omega}{\omega_c}}{1 - (\frac{\omega}{\omega_c})^2}$$

Second Order High Pass Filter

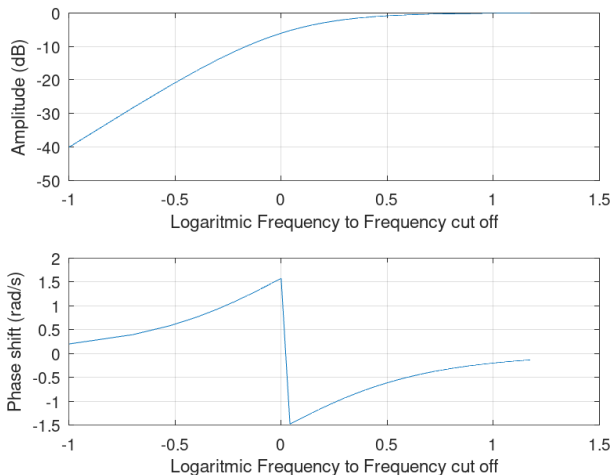Frequency response of second order active low filter.



Notch Filter/Bandstop Filter

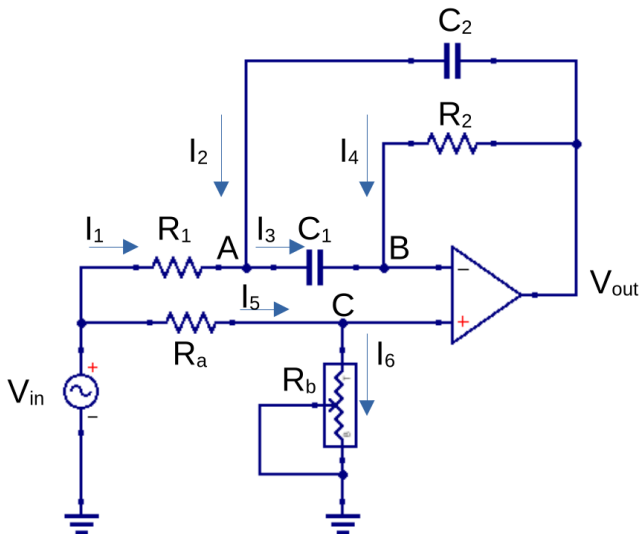

References

Floyd,T.L., Fundamentals of Analog Circuits, Prentice Hall, .

Malvino,A., Electronic Principle, McGrawHill, 2016.

Boylestad, R.L., Nashelsky,L., Electronics Devices and Circuit Theory, Pearson, 2014.

Terima Kasih