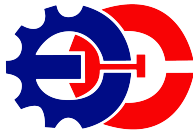


Hysteresis on Comparator

TE201414 - Rangkaian Elektronika 2

Program Studi Teknik Elektro




Institut Teknologi Kalimantan
agung.nursyeha@lecturer.itk.ac.id
miftanurfarid@lecturer.itk.ac.id


February 24, 2025

Posttest

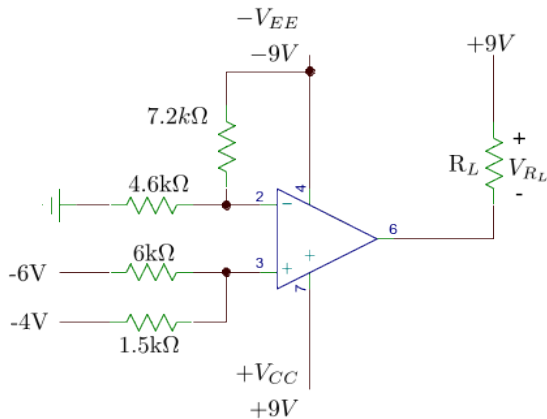
Find the voltage on Load Resistor V_{R_L}



Hysteresis

 


what if noise occurred on input op-amp?

 

it will result unwanted output voltage signal

Hysteresis

 
How to overcome this problem? by defining 2 threshold (Lower Threshold and Upper Threshold) the unwanted signal can be eliminated.



then, how is the circuit?


Hysteresis on op-amp

 by adding a connection between output and non-inverting input. the comparator circuit has 2 threshold.



Hysteresis on op-amp

while $V_{out} = +V_{CC}$, then

 


$$V_+ | V_{out} = +V_{CC} = \frac{R_2}{R_1 + R_2} (+V_{CC})$$

$V_+ | V_{out} = +V_{CC}$ is the upper threshold voltage V_{UT} , thus

$$V_{UT} = \frac{R_2}{R_1 + R_2} (+V_{CC})$$

Hysteresis on op-amp

while $V_{out} = -V_{SS}$, then

 


$$V_+|_{V_{out}=-V_{SS}} = \frac{R_2}{R_1 + R_2}(-V_{SS})$$


$V_+|_{V_{out}=-V_{SS}}$ is the lower threshold V_{LT} , thus

$$V_{LT} = \frac{R_2}{R_1 + R_2}(-V_{SS})$$


Hysteresis diagram

 

Hysteresis on op-amp

 


Hysteresis on op-amp

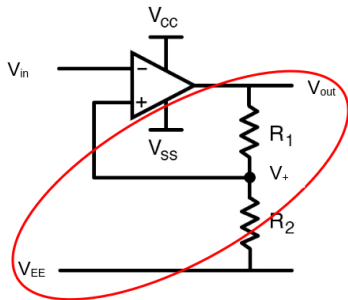

Superposition theorem is used to solve circuit problem with more than 1 sources.


Hysteresis on op-amp

 

Sumber tegangan V_{out} dimatikan, sehingga:

$$V_{+A} = \frac{R_1}{R_1 + R_2} V_{EE}$$

Hysteresis on op-amp

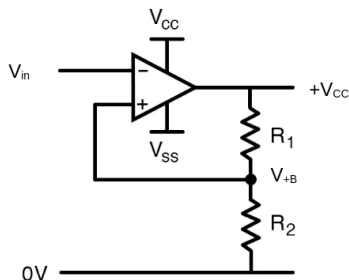

Sumber tegangan V_{EE} dimatikan,
ketika $V_{out} = +V_{CC}$:

$$V_{+B} = \frac{R_2}{R_1 + R_2} (+V_{CC})$$


Ambang batas atas V_{UT} :

$$V_{UT} = V_{+A} + V_{+B}$$

$$V_{UT} = \frac{R_1}{R_1 + R_2} (V_{EE}) + \frac{R_2}{R_1 + R_2} (+V_{CC})$$

$$V_{UT} = \frac{R_1(V_{EE}) + R_2(+V_{CC})}{R_1 + R_2}$$

Hysteresis on op-amp

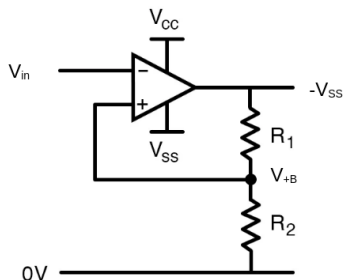

Sumber tegangan V_{EE} dimatikan,
ketika $V_{out} = -V_{SS}$:

$$V_{+B} = \frac{R_2}{R_1 + R_2}(-V_{SS})$$


Ambang batas bawah V_{LT} :

$$V_{LT} = V_{+A} + V_{+B}$$


$$V_{LT} = \frac{R_1}{R_1 + R_2}(V_{EE}) + \frac{R_2}{R_1 + R_2}(-V_{SS})$$

$$V_{LT} = \frac{R_1(V_{EE}) + R_2(-V_{SS})}{R_1 + R_2}$$

Diagram Histerisis

 


Contoh

 


Contoh

Tentukan:

 - V_{UT}
- V_{LT}
- diagram histerisis
- V_{out} apabila diberikan V_{in}




Contoh

 

Contoh

Tentukan:

 - V_{UT}
- V_{LT}
- diagram histerisis
- V_{out} apabila diberikan V_{in}



References

Boylestad, R. L., Nashelsky, L., Electronic Devices and Circuit Theory, Pearson, 2014.

Malvino, A., Bates, D., Electronic Principles, McGraw-Hill Education, 2016.

Terima Kasih